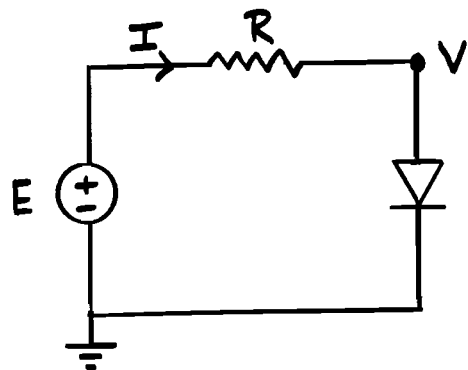


NONLINEAR PROBLEMS



$$I = \frac{E - V}{R} \quad (1)$$

ALSO, FOR THE DIODE:

$$I = I_s (e^{qV/kT} - 1) \quad (2)$$

REVERSE
SATURATION
CURRENT

$$\frac{kT}{q} \sim 25 \text{ mV} \text{ AT } 300 \text{ K}$$

NL 1

COMBINING (1) AND (2):

$$\frac{E - V}{R} = I_s (e^{qV/kT} - 1)$$

OR,

$$V = E - RI_s (e^{qV/kT} - 1)$$

NONLINEAR IN V

LET

$$f(V) \equiv V - E + RI_s (e^{qV/kT} - 1)$$

THEN, THE PROBLEM TO BE SOLVED IS:

$$f(V) = 0.$$

NL 2

SUCCESSIVE SUBSTITUTION

0. GUESS $V^{(0)}$

e.g., $V^{(0)} = 0$

SET $k = 0$

1. SOLVE FOR $V^{(k+1)}$:

$$V^{(k+1)} - E + RI_s (e^{qV^{(k)}/kT} - 1) = 0$$

OR,

$$V^{(k+1)} - V^{(k)} + f^{(k)} = 0$$

2. IF

$$f(V^{(k+1)})$$

IS SMALL ENOUGH, STOP.

ELSE:

3. SET $k = k + 1$.

GOTO 1.

NL3


SUCCESSIVE SUBSTITUTION

$E = 100 \text{ mV}$, $I_s = 1 \mu\text{A}$, $R = 500 \Omega$

k	V	f
0	0.000000	-0.100000
1	0.100000	0.026799
2	0.073201	-0.017954
3	0.091155	0.009819
4	0.081336	-0.006224
5	0.087560	0.003658
6	0.083902	-0.002259
7	0.086162	0.001356
8	0.084805	-0.000829
9	0.085634	0.000501
10	0.085133	-0.000305
11	0.085438	0.000185
12	0.085253	-0.000112
13	0.085365	0.000068
14	0.085297	-0.000041
15	0.085339	0.000025
16	0.085314	-0.000015
17	0.085329	0.000009
18	0.085320	-0.000006
19	0.085325	0.000003
20	0.085322	-0.000002
21	0.085324	0.000001
22	0.085323	-0.000001
23	0.085323	0.000000


NL4

FIG. 1 SUCCESSIVE SUBSTITUTION

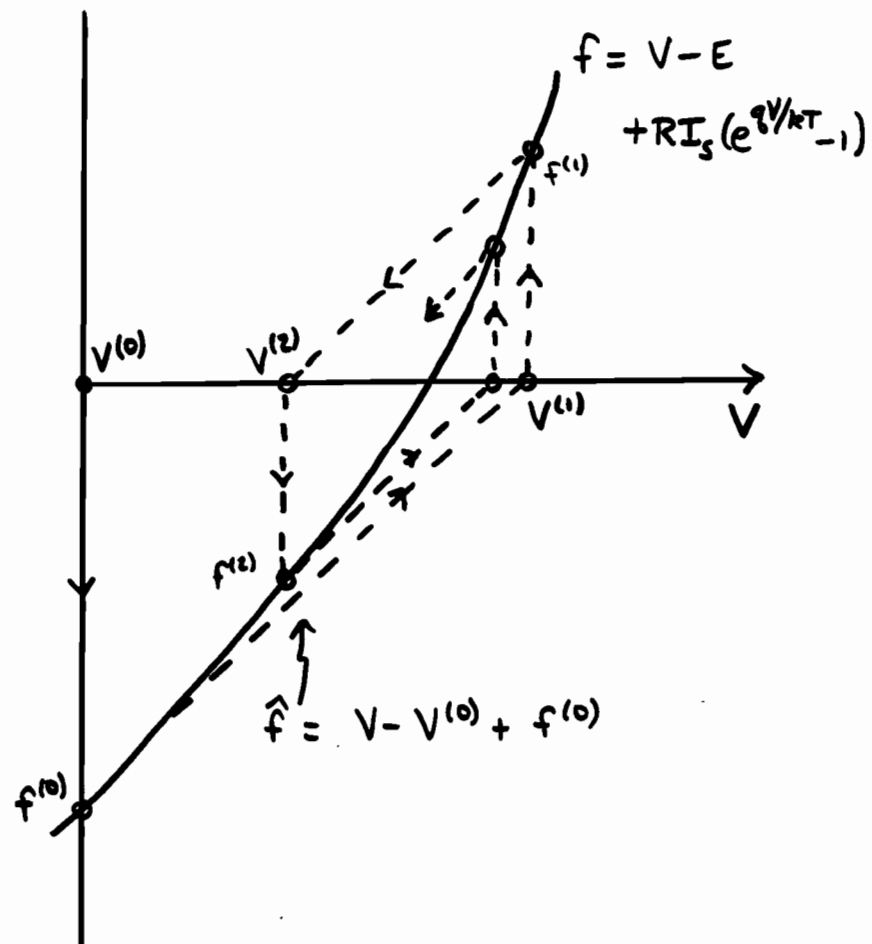

NL5

FIG. 2 NEWTON - RAPHSON

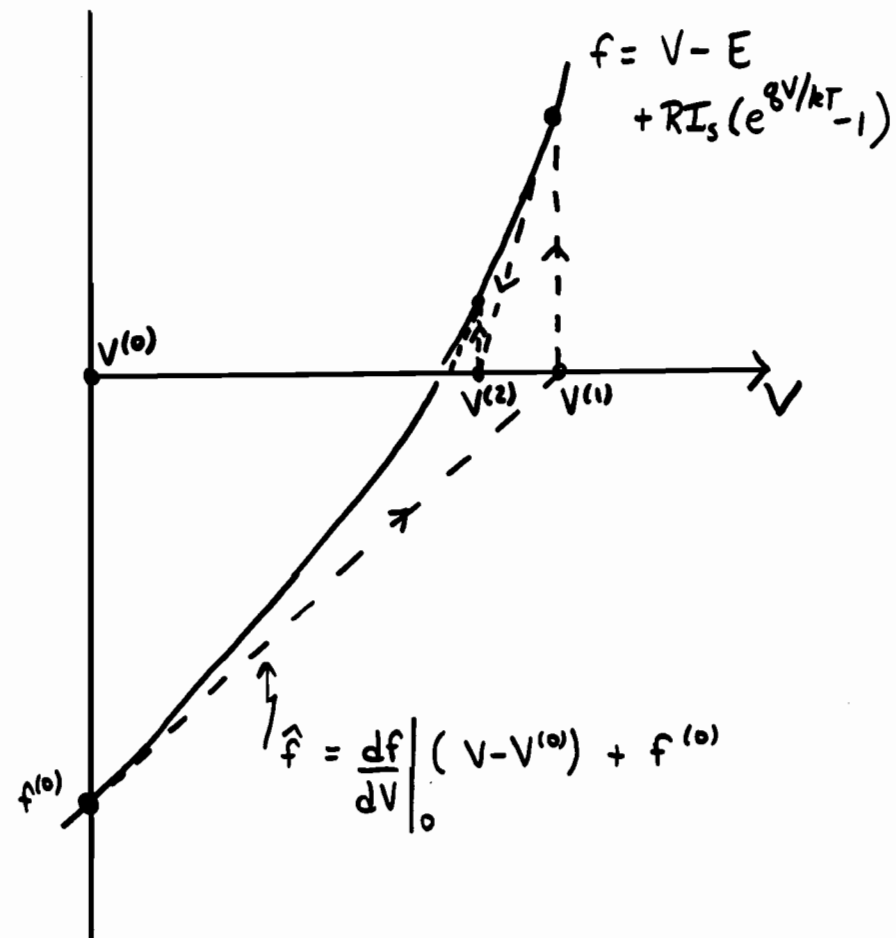

NL6

NEWTON-RAPHSON

0. GUESS $V^{(0)}$, e.g. $V^{(0)} = 0$.

SET $k = 0$.

1. SOLVE FOR $V^{(k+1)}$:

$$f'(k) (V^{(k+1)} - V^{(k)}) + f^{(k)} = 0$$

WHERE

$$f'(k) = \left. \frac{df}{dV} \right|_{V=V^{(k)}}$$

2. IF $f(V^{(k+1)})$

IS SMALL ENOUGH, STOP.

ELSE:

3. SET $k = k+1$.

GOTO 1.

NEWTON-RAPHSON

$E = 100 \text{ mV}$, $I_s = 1 \mu\text{A}$, $R = 500 \Omega$

k	V	f	f'
0	0.000000	-0.100000	1.020000
1	0.098039	0.022779	2.009591
2	0.086704	0.002243	1.641555
3	0.085338	0.000024	1.607432
4	0.085323	0.000000	1.607077

QUADRATIC CONVERGENCE :

EXPAND f IN A TAYLOR SERIES
ABOUT $V^{(k)}$:

$$f(V) = f^{(k)} + f'(k)(V - V^{(k)}) + \frac{1}{2} f''(k)(V - V^{(k)})^2 + \dots$$

IN PARTICULAR, IF $V = V_s$, THE SOLUTION:

$$\begin{aligned} f(V_s) &= f^{(k)} + f'(k)(V_s - V^{(k)}) \\ &\quad + \frac{1}{2} f''(k)(V_s - V^{(k)})^2 + \dots \end{aligned}$$

\nearrow
 $= 0$

$\underbrace{V_s - V^{(k)}}_{E_k = |V_s - V^{(k)}|}$ IGNORE CLOSE TO V_s

NL 9

THUS,

$$f^{(k)} + f'(k)(V_s - V^{(k)}) + \frac{1}{2} f''(k) E_k^2 = 0$$

DIVIDE BY $f'(k)$:

$$\frac{f^{(k)}}{f'(k)} + (V_s - V^{(k)}) + \frac{1}{2} \frac{f''(k)}{f'(k)} E_k^2 = 0$$

RE-ARRANGE :

$$V_s - \underbrace{\left(V^{(k)} - \frac{f^{(k)}}{f'(k)} \right)}_{= V^{(k+1)}} = -\frac{1}{2} \frac{f''(k)}{f'(k)} E_k^2$$

i.e.,

$$\underbrace{V_s - V^{(k+1)}}_{E_{k+1} = |V_s - V^{(k+1)}|} = -\frac{1}{2} \frac{f''(k)}{f'(k)} E_k^2$$

NL 10

OR,

$$\varepsilon_{k+1} = \frac{1}{2} \left| \frac{f''(k)}{f'(k)} \right| \varepsilon_k^2$$

IF

$$\frac{1}{2} \left| \frac{f''(k)}{f'(k)} \right| < C$$

THEN

$$\varepsilon_{k+1} < C \varepsilon_k^2 .$$

SUPPOSE


$$\varepsilon_k = 10^{-n}$$

THEN

$$\varepsilon_{k+1} < C 10^{-2n} .$$

NL //

NONLINEAR NETWORKS

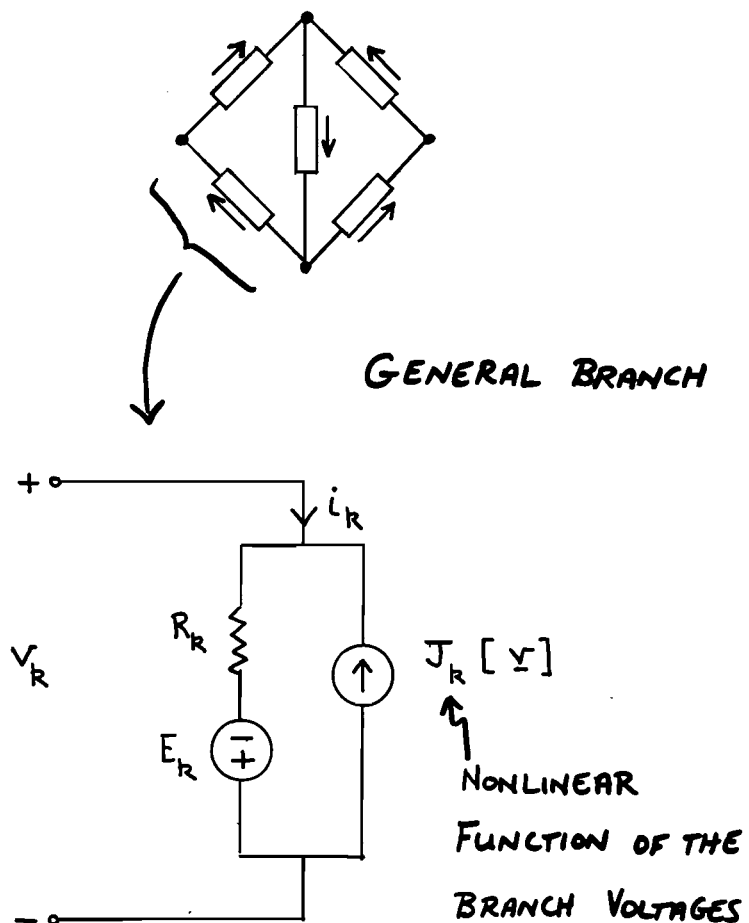

NL 12

e.g., DIODE :

$$J_k = -J_s (e^{qV_k/kT} - 1)$$

NETWORK EQUATIONS :

KCL : $\underline{A} \underline{i} = 0$ ← REDUCED INCIDENCE MATRIX

KVL : $\underline{v} = \underline{A}^T \underline{v}_n$ ← NODAL VOLTAGES

BRANCH

EQUATIONS : $\underline{i} = \underline{Y} \underline{v} + \underline{Y} \underline{E} - \underline{J}[\underline{v}]$

COMBINING :

$$(\underline{A} \underline{Y} \underline{A}^T) \underline{v}_n = \underline{A} (\underline{J}[\underline{A}^T \underline{v}_n] - \underline{Y} \underline{E})$$

↑ NONLINEAR IN \underline{v}_n

NL 13

LET

$$\underline{f}[\underline{v}_n] \equiv (\underline{A} \underline{y} \underline{A}^T) \underline{v}_n$$

$$- \underline{A} \underline{J}[\underline{A}^T \underline{v}_n] + \underline{A} \underline{y} \underline{E}$$

THEN THE PROBLEM TO BE SOLVED IS:

$$\underline{f}[\underline{v}_n] = 0$$

SUCCESSIVE SUBSTITUTION:

\Rightarrow AT EACH STEP, HOLD $\underline{J}[\underline{A}^T \underline{v}_n]$
FIXED AND SOLVE A LINEAR
PROBLEM.

SUCCESSIVE SUBSTITUTION

0. GUESS $\underline{v}_n^{(0)}$, e.g., $\underline{v}_n^{(0)} = 0$

SET $k = 0$.

1. SOLVE FOR $\underline{v}_n^{(k+1)}$:

$$(\underline{A} \underline{y} \underline{A}^T) \underline{v}_n^{(k+1)} = \underline{A} \underline{J}[\underline{A}^T \underline{v}_n^{(k)}] \\ - \underline{A} \underline{y} \underline{E}$$

OR,

$$(\underline{A} \underline{y} \underline{A}^T) (\underline{v}_n^{(k+1)} - \underline{v}_n^{(k)}) + \underline{f}^{(k)} = 0$$

2. IF $\underline{f}^{(k+1)}$ IS SMALL ENOUGH, STOP.
ELSE:

3. SET $k = k+1$. GOTO 1.

TO GET NEWTON-RAPHSON, REPLACE:

$$(\underline{A} \underline{Y} \underline{A}^T) (\underline{v}_n^{(k+1)} - \underline{v}_n^{(k)}) + \underline{f}^{(k)} = 0$$

BY:

$$\underbrace{\frac{d\underline{f}^{(k)}}{d\underline{v}_n}}_{\text{JACOBIAN MATRIX } \underline{J}^{(k)}} (\underline{v}_n^{(k+1)} - \underline{v}_n^{(k)}) + \underline{f}^{(k)} = 0$$

JACOBIAN MATRIX $\underline{J}^{(k)}$

$$J_{ij}^{(k)} = \left. \frac{\partial f_i}{\partial v_{nj}} \right|_{\underline{v}_n = \underline{v}_n^{(k)}}$$

RECALL,

$$\underline{f} = (\underline{A} \underline{Y} \underline{A}^T) \underline{v}_n - \underline{A} \underline{J} [\underline{A}^T \underline{v}_n] + \underline{A} \underline{Y} \underline{E}$$

Thus,

$$\begin{aligned} \frac{\partial \underline{f}}{\partial \underline{v}_n} &= (\underline{A} \underline{Y} \underline{A}^T) - \underline{A} \underbrace{\frac{\partial \underline{J}}{\partial \underline{v}_n}}_{\downarrow} \\ &= \frac{\partial \underline{J}}{\partial \underline{v}} \underbrace{\frac{\partial \underline{v}}{\partial \underline{v}_n}}_{\downarrow} \\ &= \frac{\partial}{\partial \underline{v}_n} (\underline{A}^T \underline{v}_n) = \underline{A}^T \end{aligned}$$

HENCE,

$$\underline{\underline{J}} = \frac{\partial \underline{f}}{\partial \underline{v}_n} = (\underline{\underline{A}} \underline{\underline{Y}} \underline{\underline{A}}^T) - \underline{\underline{A}} \frac{\partial \underline{J}}{\partial \underline{v}} \underline{\underline{A}}^T$$

\uparrow
 AVAILABLE
 FROM DEVICE
 CHARACTERISTICS


SUCCESSIVE SUBSTITUTION:

$$(\underline{\underline{A}} \underline{\underline{Y}} \underline{\underline{A}}^T) (\underline{v}_n^{(k+1)} - \underline{v}_n^{(k)}) + \underline{f}^{(k)} = 0$$

NEWTON-RAPHSON:



$$(\underline{\underline{A}} \underline{\underline{Y}} \underline{\underline{A}}^T - \underline{\underline{A}} \frac{\partial \underline{J}}{\partial \underline{v}} \underline{\underline{A}}^T) (\underline{v}_n^{(k+1)} - \underline{v}_n^{(k)}) + \underline{f}^{(k)} = 0.$$

TRANSISTOR (EBERS-MOLL):

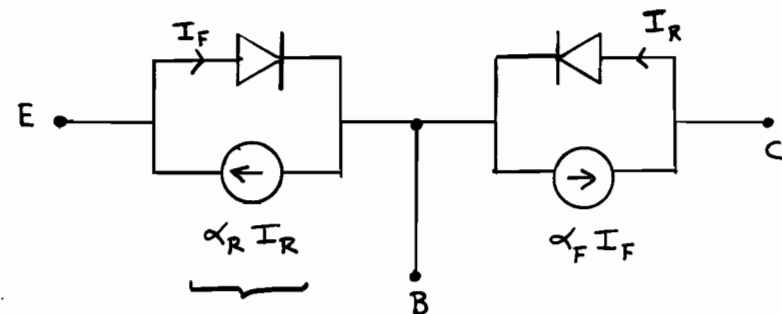


DEPENDENT
CURRENT SOURCE

MAGNETIC CIRCUITS

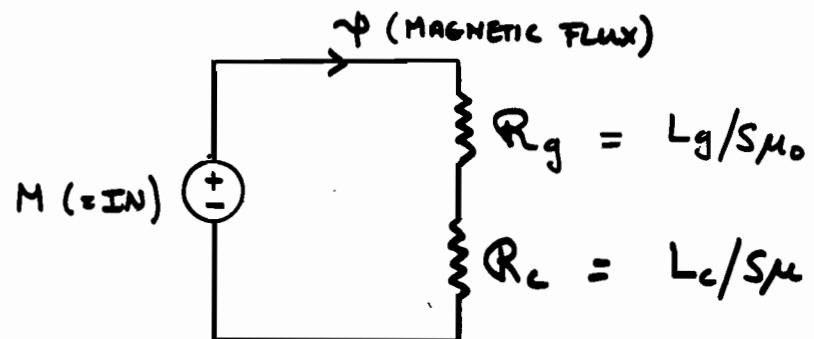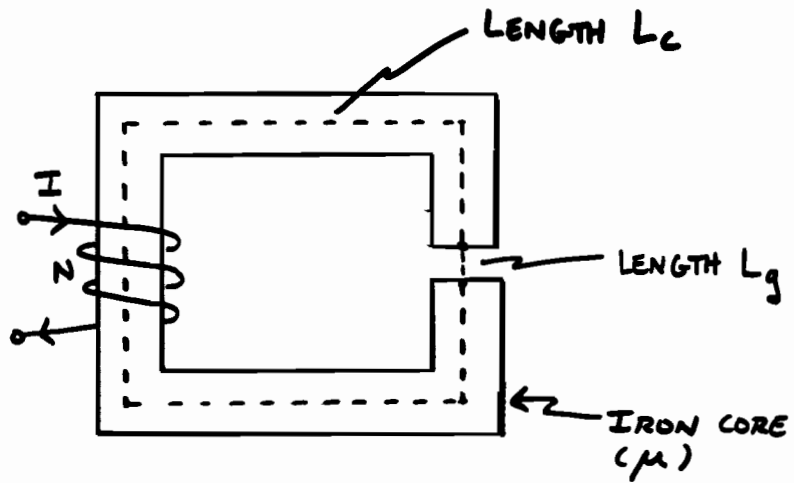

$$\Rightarrow (R_g + R_c)\psi = M$$

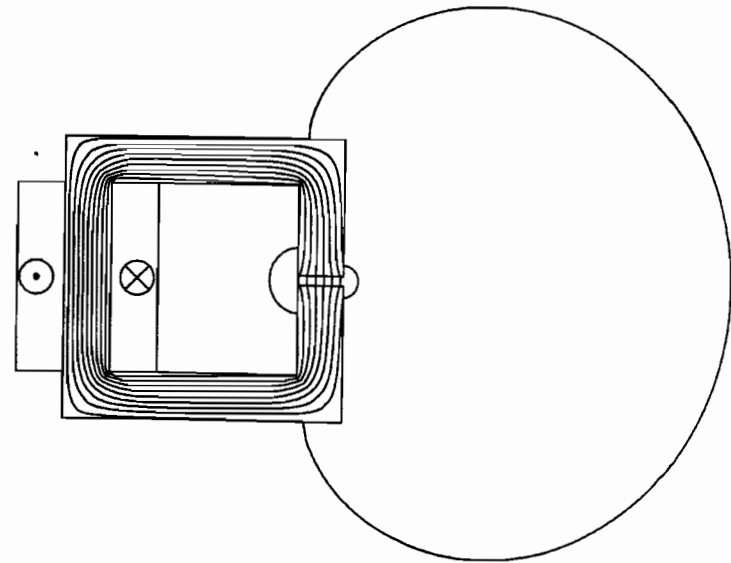

$$(R_g + R_c) \psi = M$$


$$R_c = \frac{L_c}{S\mu}$$

$$\mu = \frac{B}{H}$$

$$= \mu(B)$$

$$B = \text{FLUX DENSITY}$$

$$= \psi/S$$

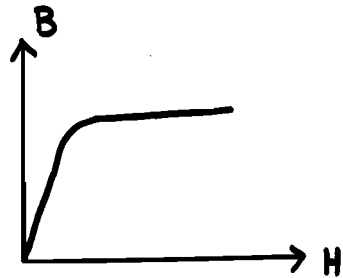

THUS,

$$(R_g + R(\psi)) \psi = M$$

NONLINEAR IN ψ